
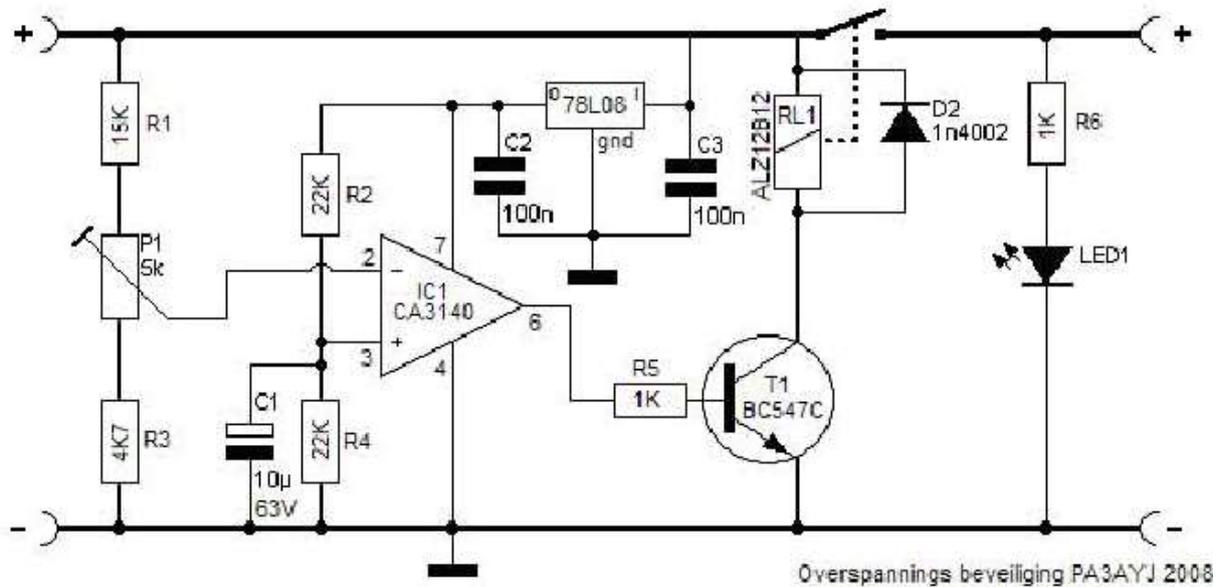



Overvoltage protector

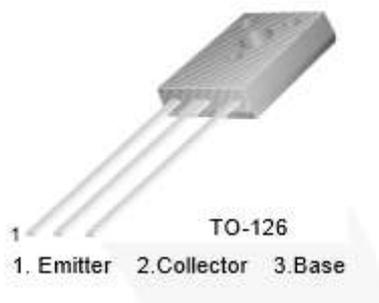

Switching transistor T1 (for example BD135) for switching car relays (with larger coil current)



Car Relay 40A instead of standard RL1

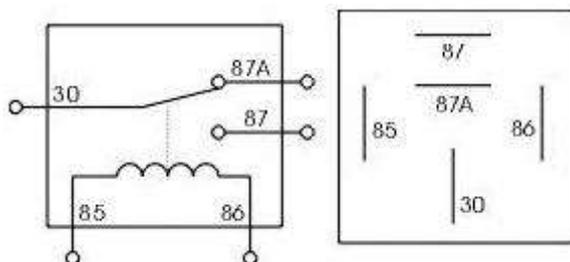

85 and 86 Coil 12V

30 = V in (from regulator)

87 = V out (to equipment)