


Controller for 70cm PA with MRF6VP3450H by ON1BTE

I am using 3 Fans (230VAC). I've build a fan speed regulator which is controlled by the PWM output from the Arduino. The higher the temperature, the higher the fan speed.
The Arduino measures the temperature, the current, 50V power supply and the bias.
The Arduino could also disable the bias. Scheme attached at the end of this document.


3x 230VAC Fan, Fan Speed Regulator (middle) en 10VDC (left) - to make 5VDC with




70cm PA, Controller and LCD.

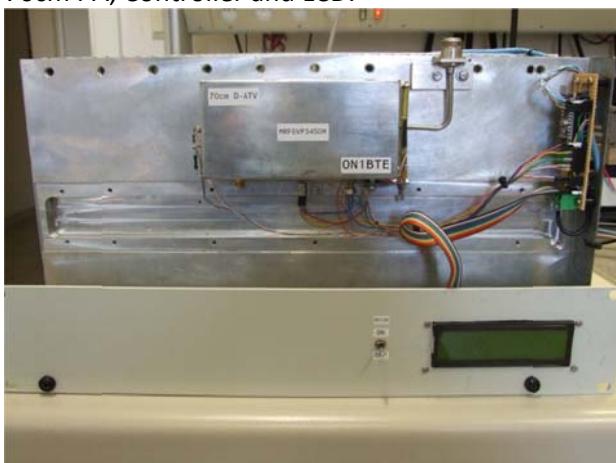


Inside the PA.

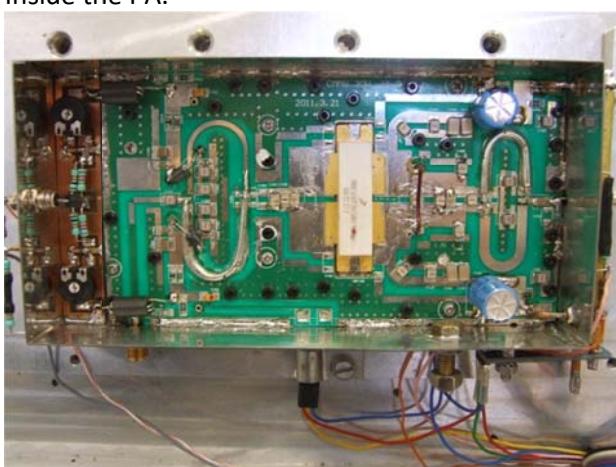

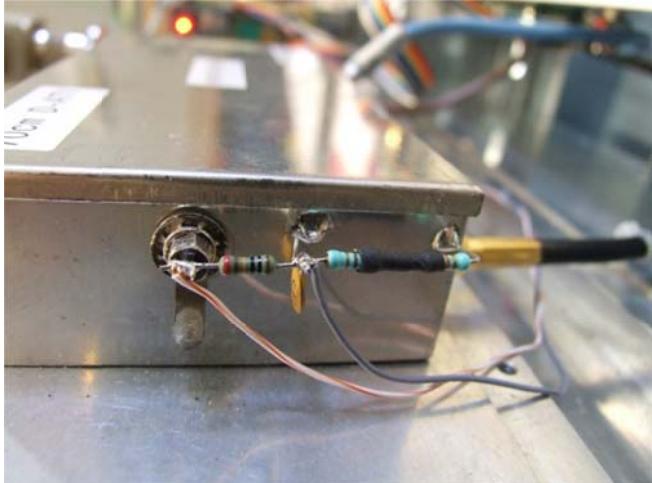
Ubias (50VDC) measuring (divider → :10,24)



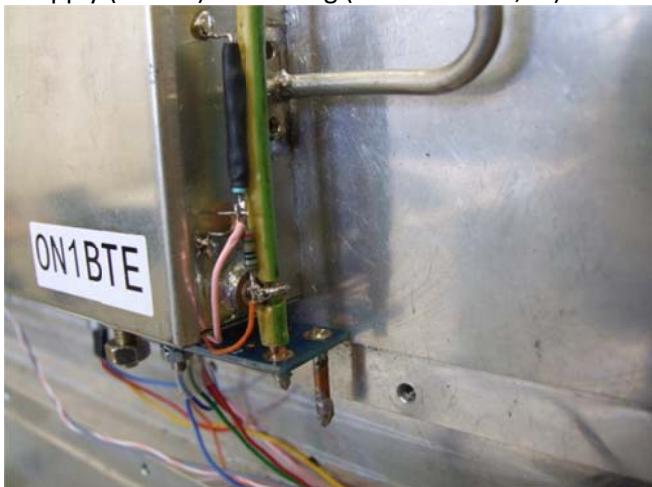Usupply (50VDC) measuring (divider → :10,24)



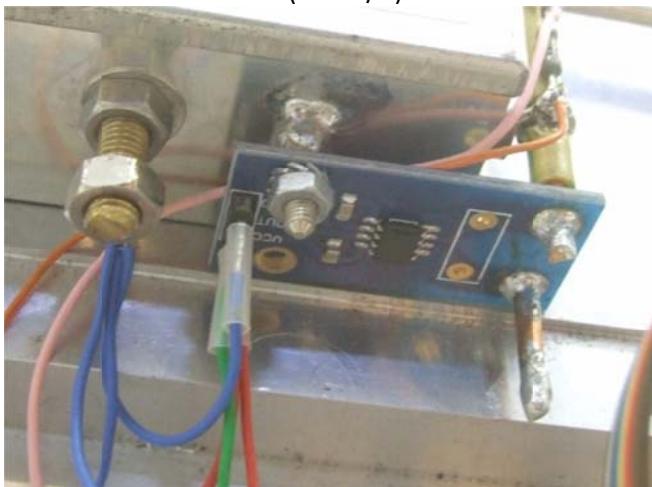
Current Sensor ACS712 (66mV/A) – max 30A.



Temperature sensor DS18B20



Controller board (Arduino ProMini)

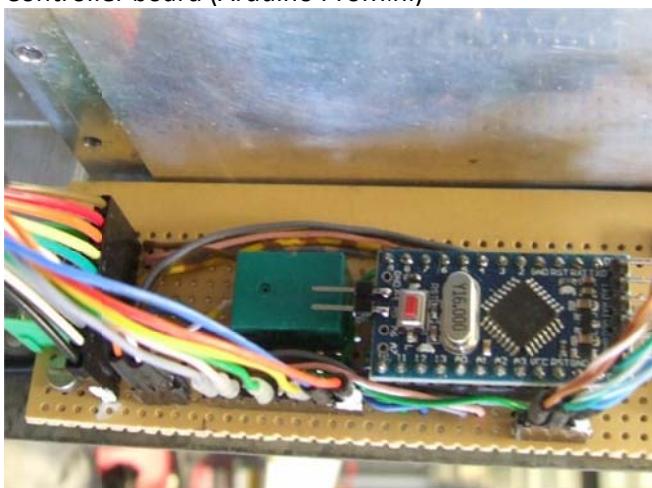

LCD (Rear) and Bias On/Off switch



Startup





PA in action ... ^ → Bias On * → Fan On



If you want the Arduino Sketch ...


E-mail to: on1bte@telenet.be

Pinouts:
Pin 1: +5V

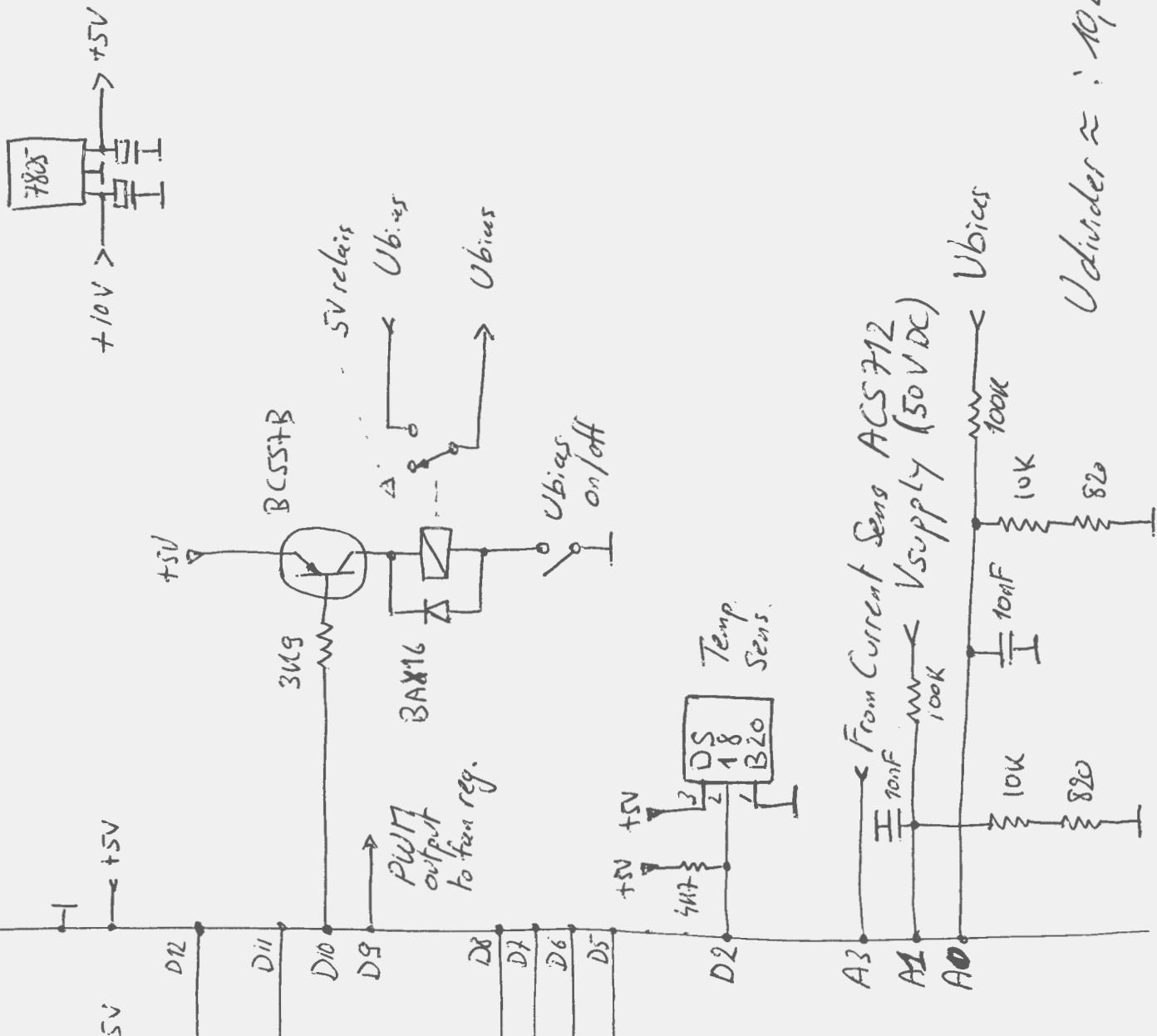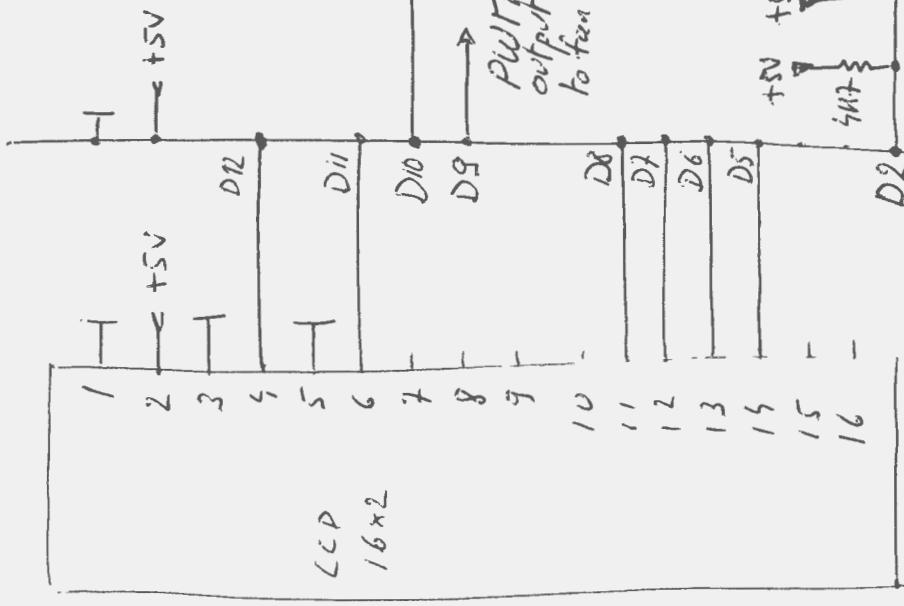


ON1BT
4/11/2017
MRF6UP3550H
Controller
Divider $\approx 10^{24}$

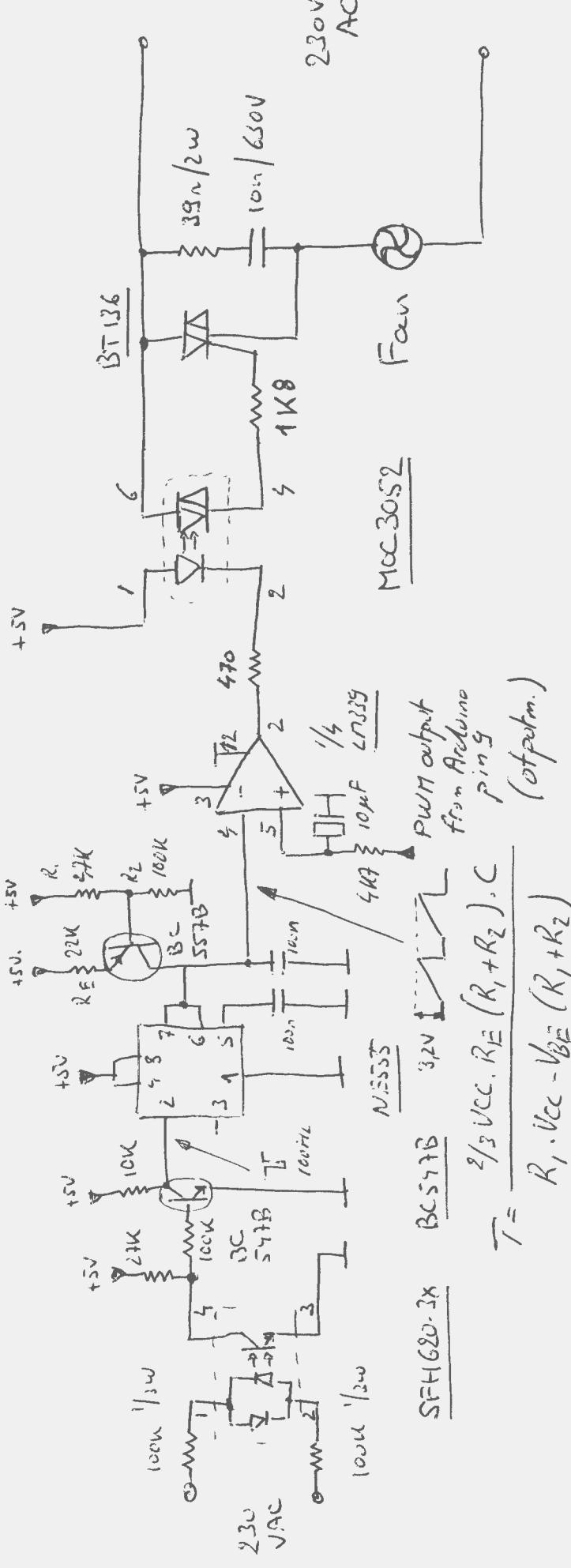Nuldoorgangsdetectie Rampgenerator Comparator
Triac starting



Fan Speed Regulator (230VAC)

ON/BIKE
4/11/2017

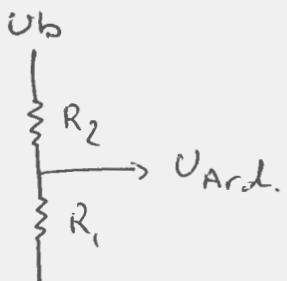

$$U_{Ard} = U_b \cdot \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{U_{Ard}}{U_b} = \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{5}{51,2} = \frac{1}{10,24}$$

$$\text{of } R_1 = \frac{R_2}{51,24}$$


$$U_b \quad R_2 = 100K \quad R_1 = 10,8225K$$

Arduno Input max 5V

$$0V \rightarrow 0$$

$$5V \rightarrow 1023$$
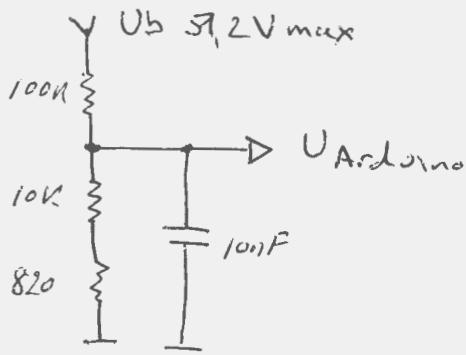
$$1\text{step} = 50mV \Rightarrow 1024\text{steps} = 51,2V (\max)$$



$$51,2 \cdot \frac{10820}{110820} = 4,99895V$$

Voor 50V

$$50 \cdot \frac{10820}{110820} = 4,8818V \quad (\rightarrow 999,79)$$